

ЦИФРОВА СХЕМОТЕХНІКА

ЗАНЯТТЯ 5. ЛІЧИЛЬНИКИ, ЧАСОВІ ЗАТРИМКИ, ФОРМУВАННЯ
ТРИВАЛОСТІ ІМПУЛЬСУ



ЛІЧИЛЬНИКИ, ЧАСОВІ ЗАТРИМКИ, ФОРМУВАННЯ ТРИВАЛОСТІ ІМПУЛЬСУ

Лічильники, часові затримки та формувачі імпульсів — це ключові елементи цифрової схемотехніки, що використовуються в різних електронних пристроях для синхронізації, вимірювання часу, обробки сигналів і управління процесами.

Лічильники (Counter) — цифрові пристрої, що рахують імпульси та можуть зберігати кількість вхідних тактових сигналів. Вони бувають зростаючими (**up-counter**), спадаючими (**down-counter**) або двонаправленими (**up/down-counter**) з керуючим сигналом.


За способом організації зміни станів:

Асинхронний (Ripple Counter) — кожен тригер змінює свій стан після зміни попереднього, що спричиняє затримку (накопичення затримки з кожним бітовим розрядом).

Синхронний (Synchronous Counter) — усі тригери змінюють стан одночасно, що зменшує затримку та підвищує швидкодію.

Лічильники використовуються в цифрових системах для:

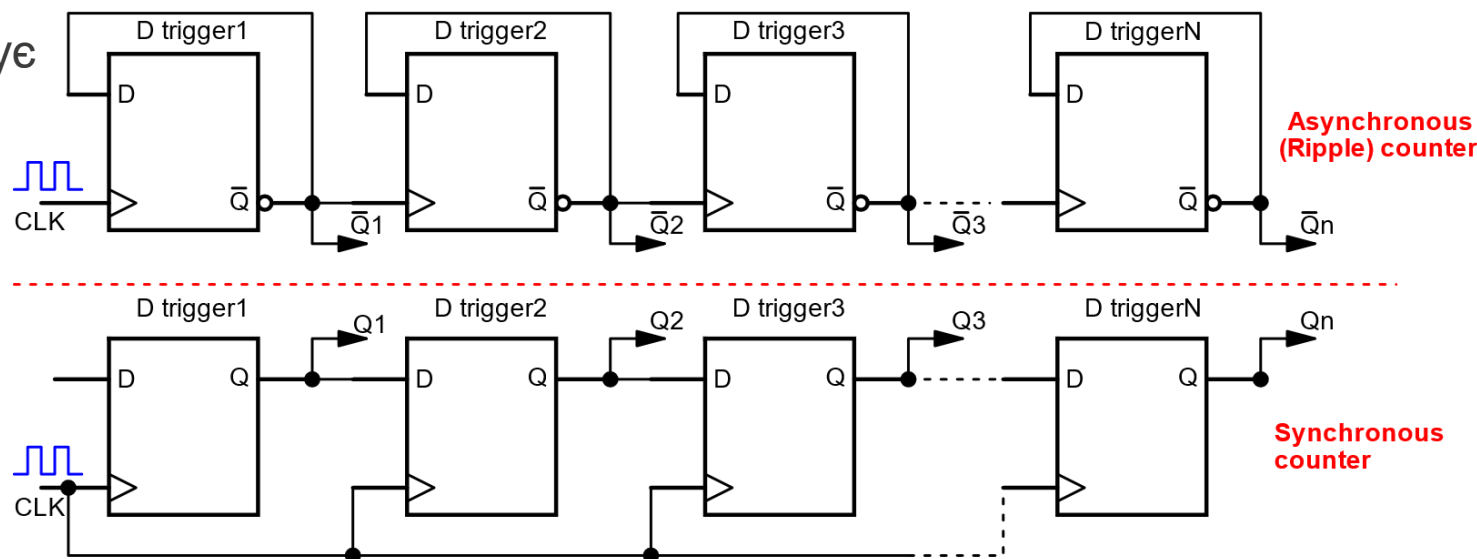- Вимірювання часу та частоти
- Синхронізації процесів
- Адресації в пам'яті
- Керування послідовностями дій





COUNTERS

1-BIT, 2-BITS, 3-BITS COUNTER

Почнемо ще раз з початку, а саме з Д тригера зі зворотнім зв'язком nQ на D.

Кожного разу при наростаючому рівні на вході CLK, стан вихіді nQ змінюється на протилежний $1 \rightarrow 0 \rightarrow 1 \rightarrow 0 \dots$

 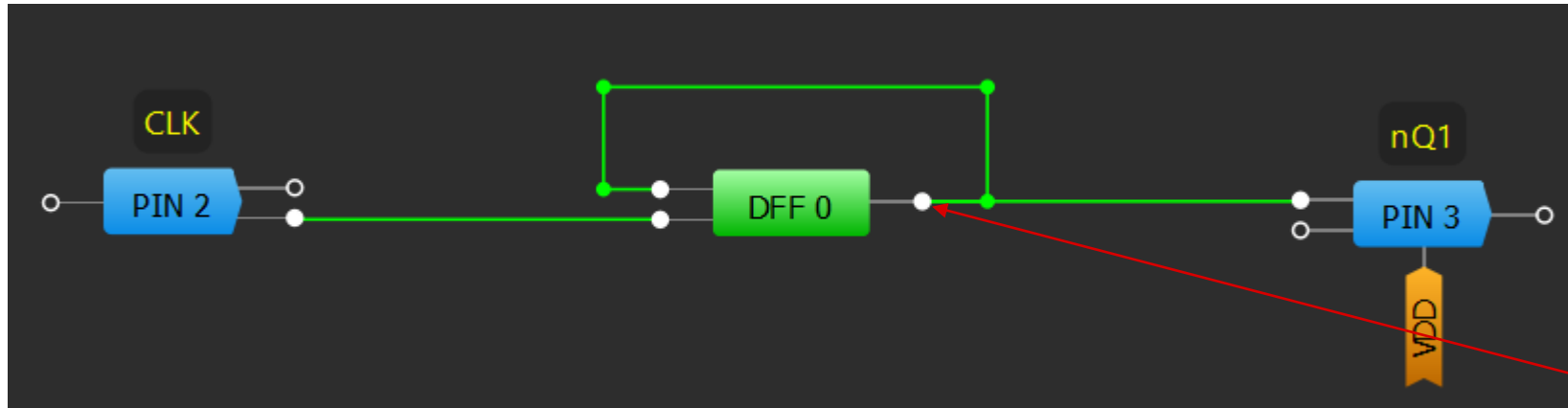Ця операція називається Toggle (див. заняття про T і JK тригери)



Properties

2-bit LUT0/DFF/LATCH0

Type: DFF / LATCH

Mode: DFF

Second Q select: None

nSET/nRESET option: None

Initial polarity: Low

Q output polarity: **Inverted (nQ)**

Information


Normal operation

D	CLK	Q(t)	nQ(t)
0	↑	0	1
0	↓	t - 1	t - 1
1	↑	1	0
1	↓	t - 1	t - 1

t - 1 - previous state;



1-BIT, 2-BITS, 3-BITS COUNTER


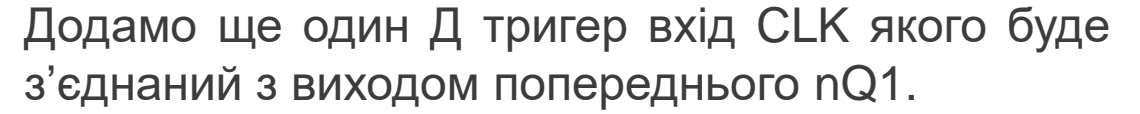


Отже, зміна стану nQ1 по наростаючому фронту буде спричиняти зміну стану nQ2





COUNTERS

1-BIT, 2-BITS, 3-BITS COUNTER

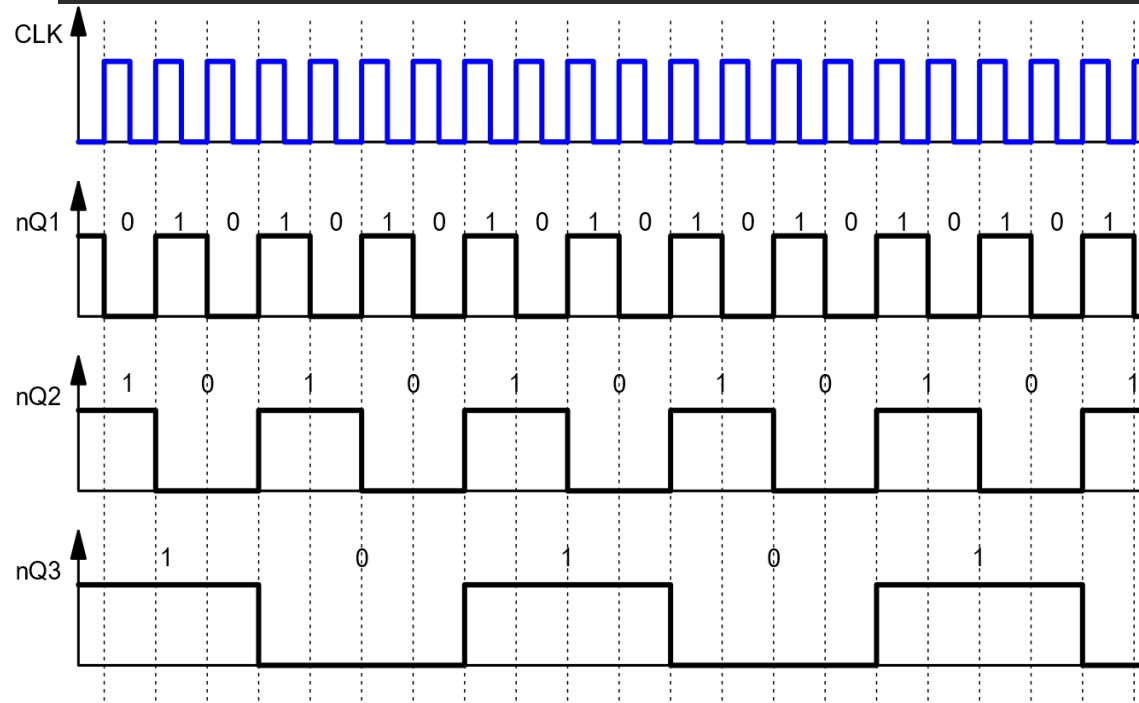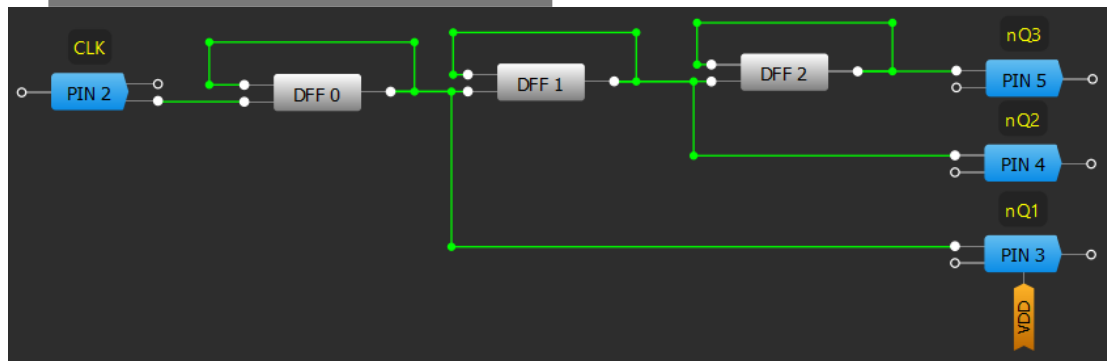


Як завжди ускладнюємо 😊

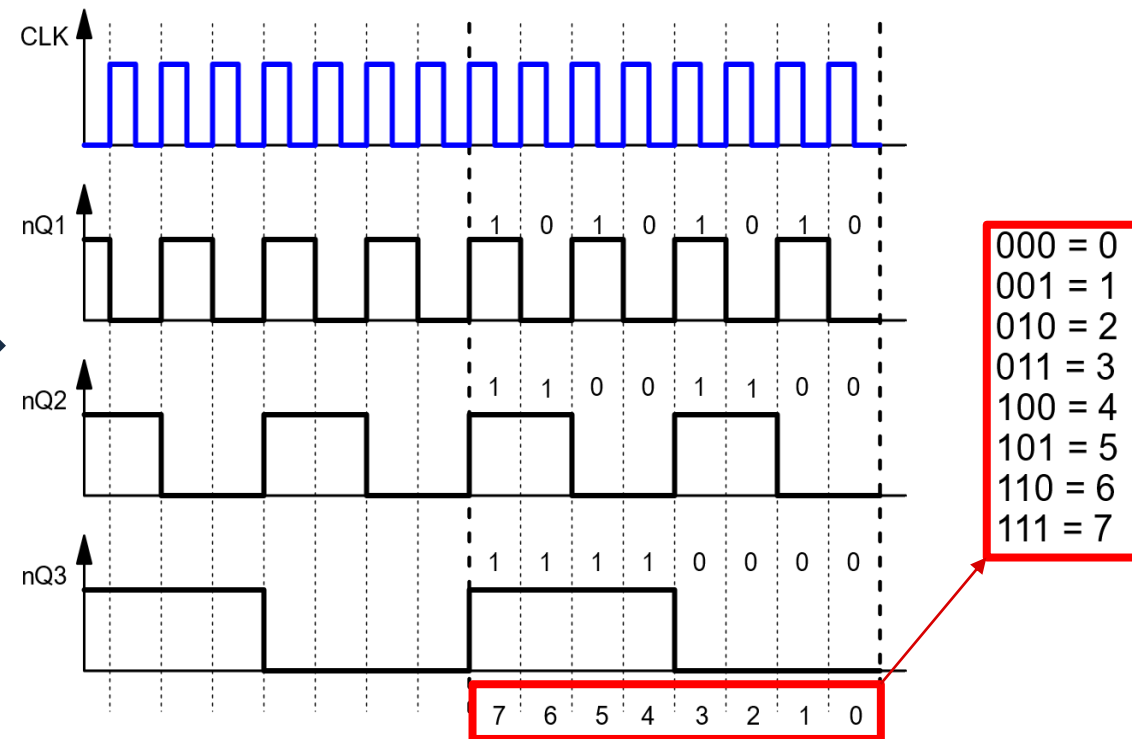 Додамо ще один Д тригер вхід CLK якого буде з'єднаний з виходом попереднього nQ2.



COUNTERS

1-BIT, 2-BITS, 3-BITS COUNTER

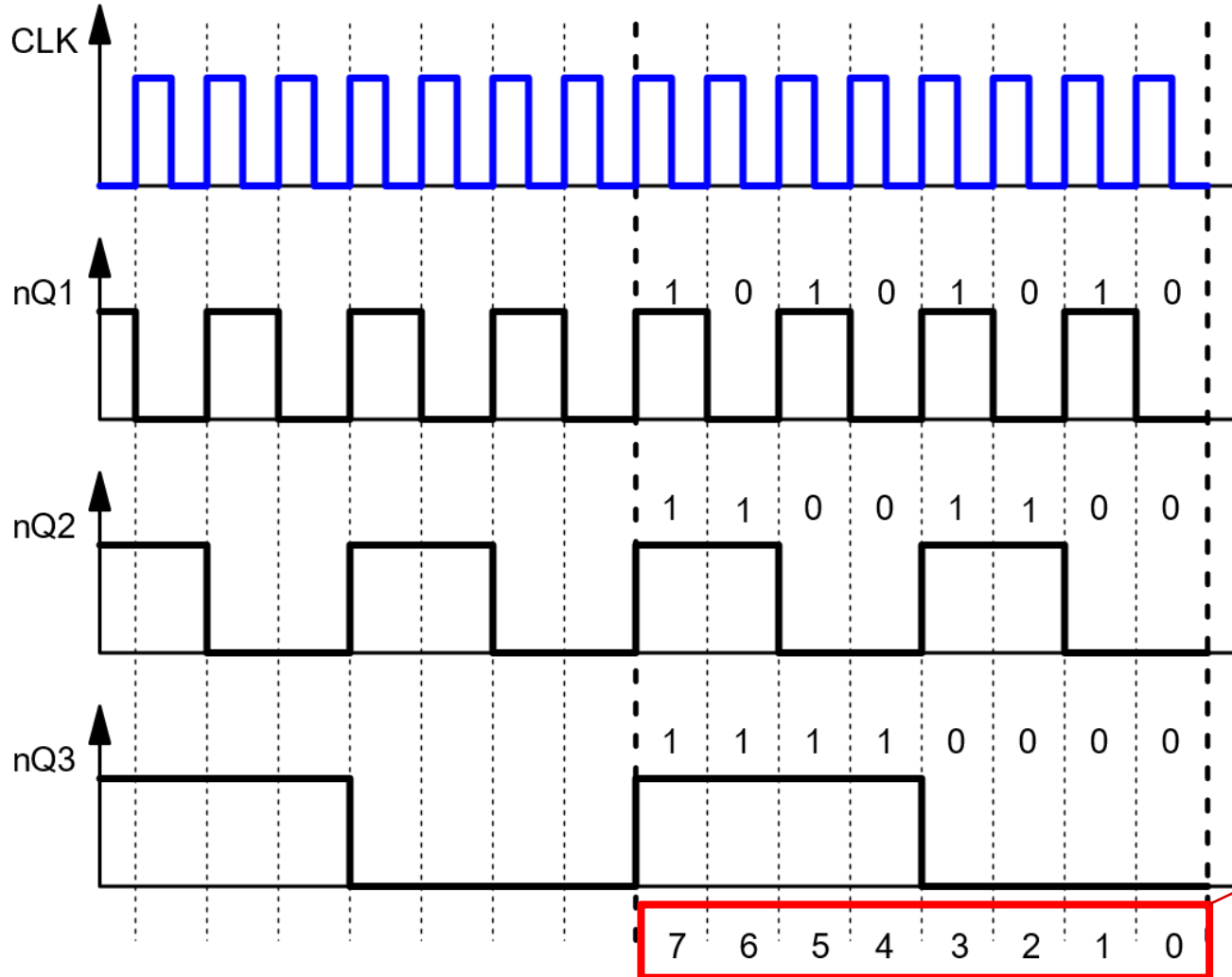

Висновок:

1. 3-бітним асинхронним лічильником, можна циклічно рахувати від 0 до 7.

2. Вхідна частота CLK буде ділитися на 2^N , N – кількість послідовно підключених Д тригерів. $F_{Qn} = F_{clk} / 2^N$


000	=	0
001	=	1
010	=	2
011	=	3
100	=	4
101	=	5
110	=	6
111	=	7

Ліричний відступ в сторону, щоб
поговорити про практичну роботу 😎

COUNTERS. HOMEWORK EXAMPLE

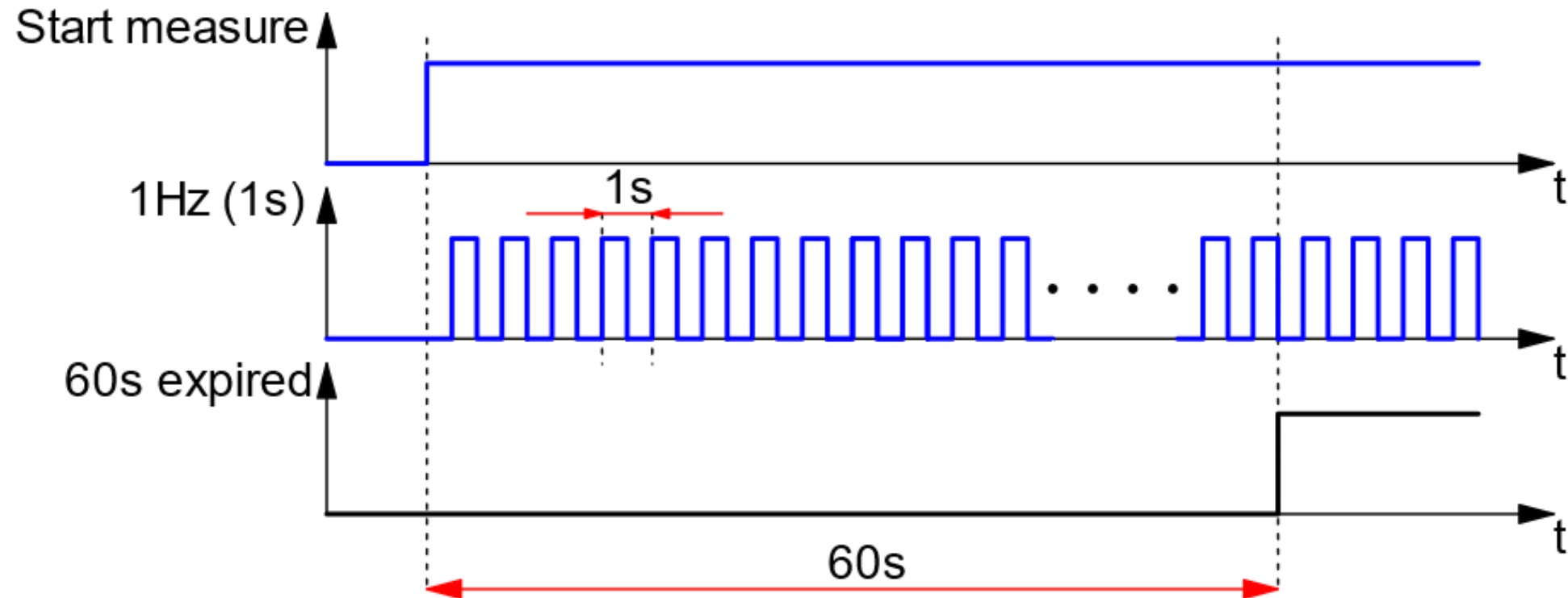Приклад, який дасть (принаймі, я так задумував) додаткове розуміння, як робити практичну роботу №4


Уявимо, що на вхід лічильника приходить частота 1Hz (період $T=1\text{s}$, як в звичайному годиннику😊). Спробуємо зробити затримку на 1хв



COUNTERS. HOMEWORK EXAMPLE



60s delay.gp6

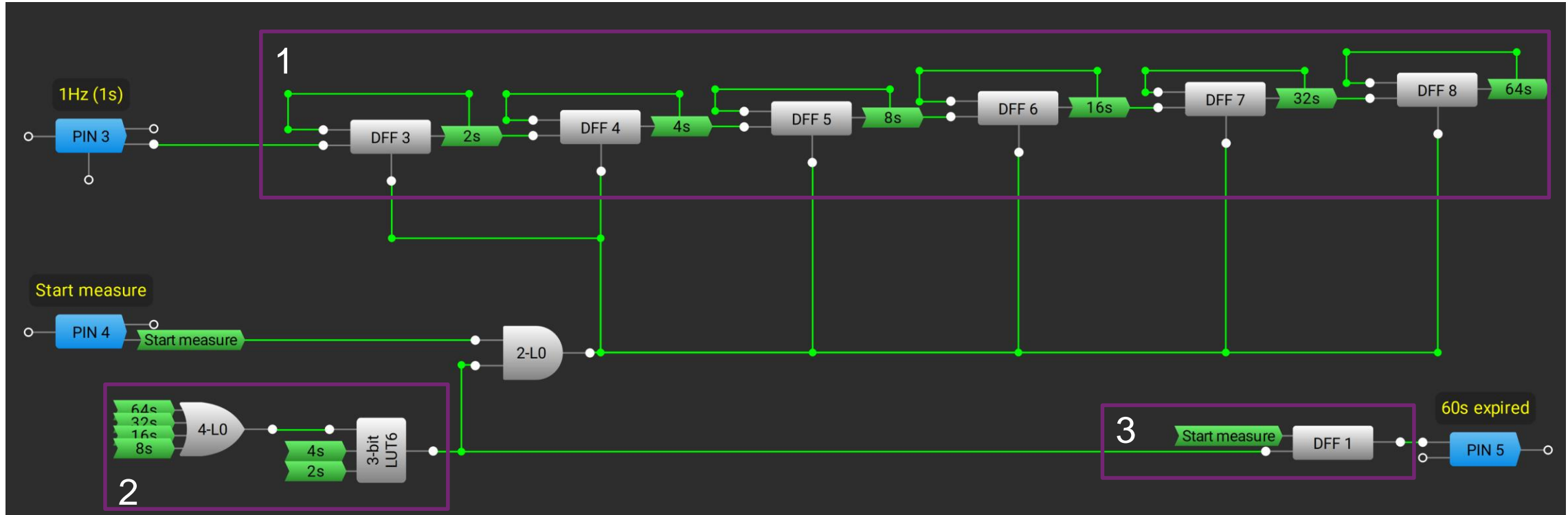


1. Асинхронний лічильник до 2^6
2. Декодер числа 60 і умова скидання лічильника
3. Запам'ятовування стану **60s expired**

Вертаємось назад до теми заняття 😎

COUNTERS

RIPPLE COUNTER IN GPAK

 1. Може рахувати, як вниз, так і ввверх, динамічно змінюючи напрямок рахунку
2. Два режими роботи – **RANGE** (лічильник рахує між SV та EV) та **FULL** (лічильник переходить через 0 і продовжує рахунок від EV).



Properties

3-bit LUT6/Pipe Delay/Ripple Counter


Type: Ripple Counter

nSET value (SV): 0

End value (EV): 0

Functionality mode: Full: 0-EV/EV-0 cyc

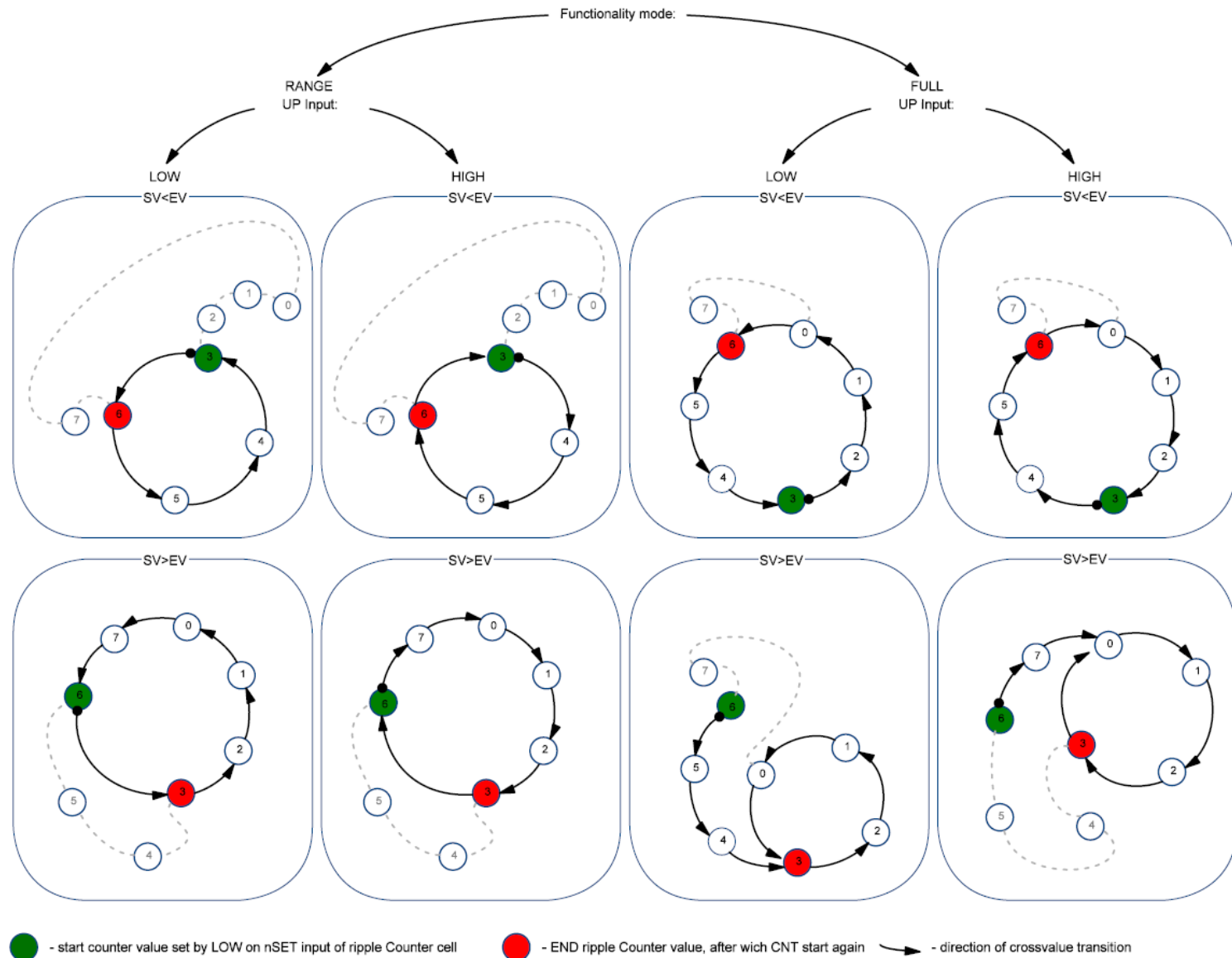
000 = 0
 001 = 1
 010 = 2
 011 = 3
 100 = 4
 101 = 5
 110 = 6
 111 = 7




PGEN

PGEN генерує повторюваний рядок до 16 бітів, які змінюються передній фронт тактового сигналу.

 Може бути використаний, як дільник частоти 😊 до 16



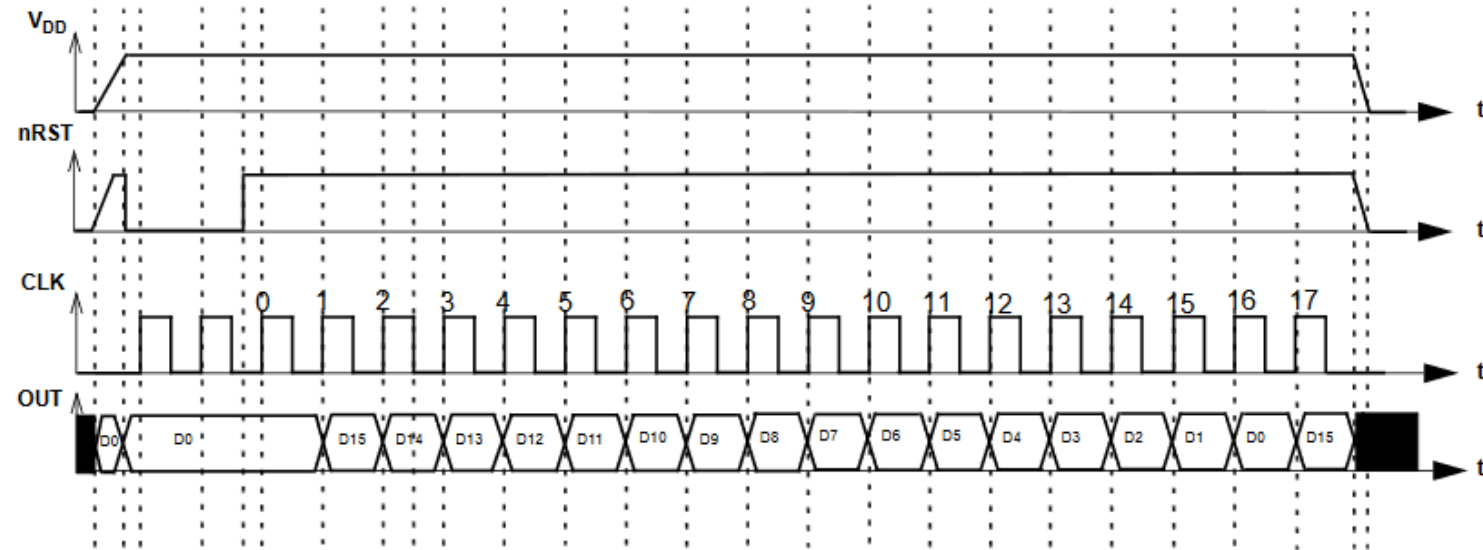
- Якщо на виводі nRESET є сигнал HIGH, PGEN згенерує рядок бітів, в іншому випадку він збереже стан 0-біт
- **Bit range** задає кількість бітів в послідовності
- **Pattern** задає саму послідовність
- Можливість змінити активний рівень для RST/SET



Properties	
2-bit LUT2/PGEN	
Type:	PGEN
Bit range:	15 : 0
Pattern:	0000000001010000
Active level for RST/SET:	Low level
<div><div><div></div><div></div><div></div></div><div>Apply</div></div>	

COUNTER DELAY (CNT/DLY) BLOCKS

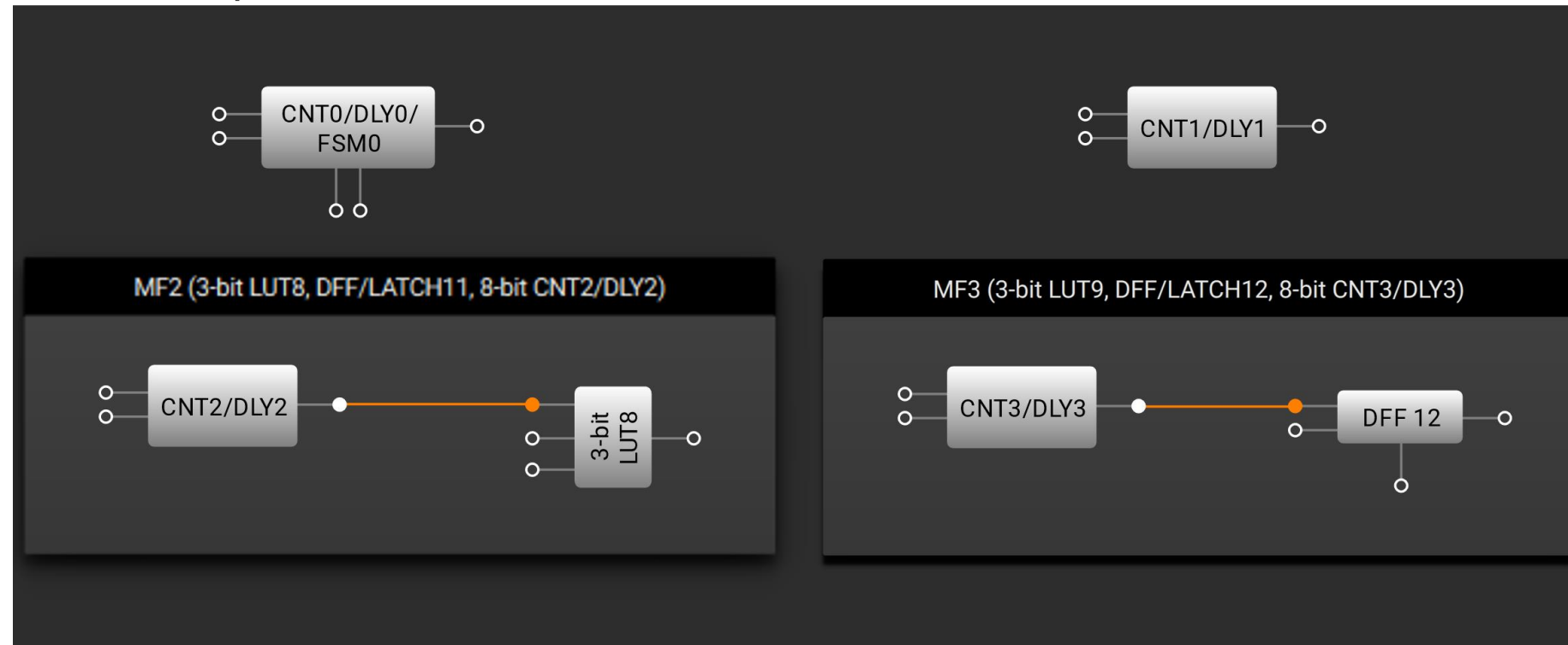- CNT/DLY macrocells allow diverse customization of timing sequences
- Configuration modes to match unique behavior
 - Delay
 - One-shot
 - Frequency Detect
 - Reset Counter
 - Edge Detect
 - Delayed Edge Detect



CNT/DLY BLOCK ON EXAMPLE SLG46826

DELAY MODE

Properties

8-bit CNT1/DLY1 (MF1)

Multi-function mode: CNT/DLY

Mode: Delay

Counter data: 1
(Range: 1 - 255)

Delay time (typical): 976.563 ns
[Formula](#)

Edge select: Both

DLY IN init. value: Bypass the initial

Output polarity: Non-inverted (OUT)

Up signal sync.: None

Keep signal sync.: None

Mode signal sync.: Bypass

Connections

Clock: OSC1

Clock source: OSC1 Freq.

Clock frequency: 2.048 MHz



Counter data: 255
(Range: 1 - 255)


Delay time (typical): 125 us
[Formula](#)

Bypass the initial

Initial 0

Initial 1

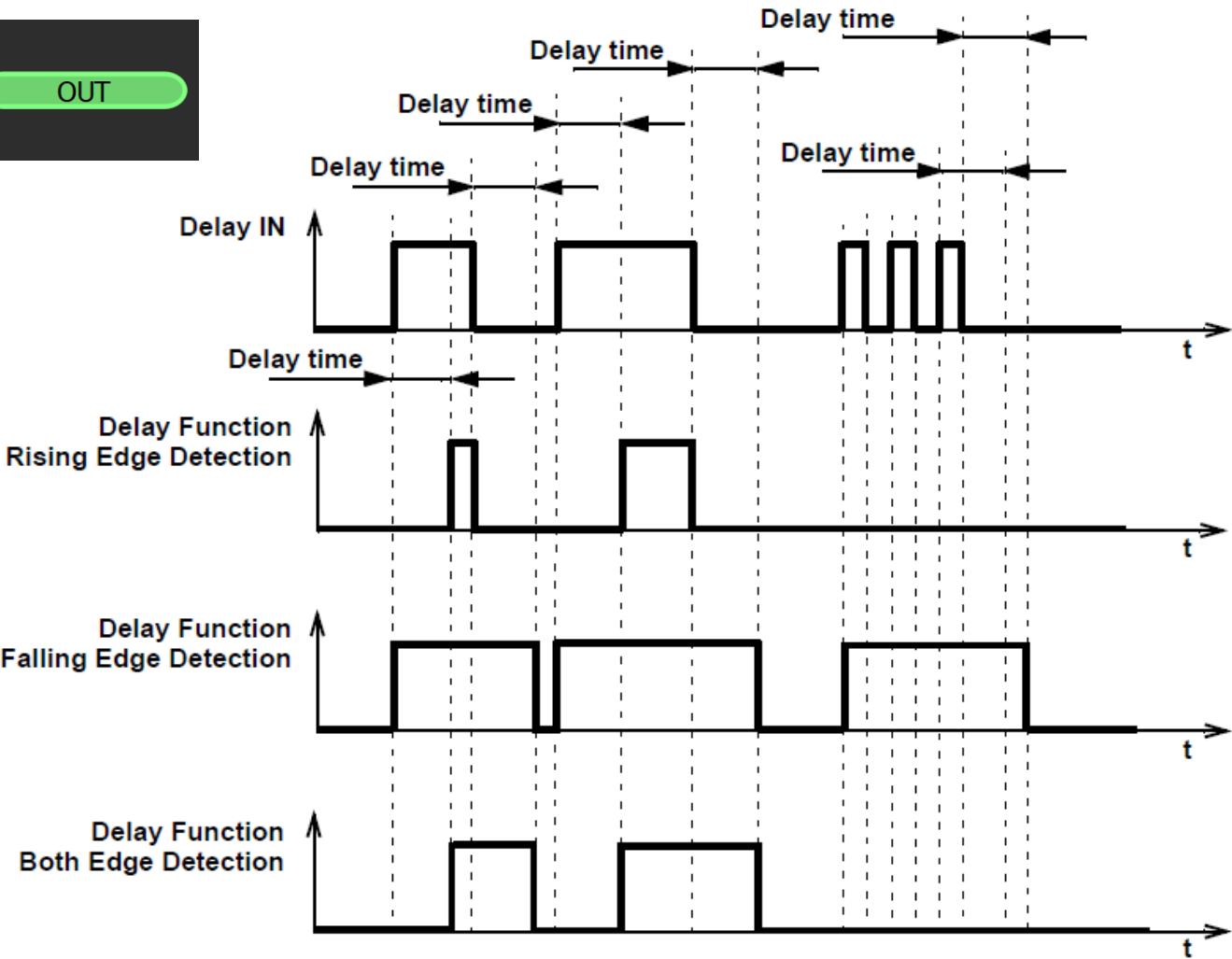- OSC2
- OSC2 /4
- OSC1
- OSC1 /8
- OSC1 /64
- OSC1 /512
- OSC0
- OSC0 /8
- OSC0 /64
- OSC0 /512
- OSC0 /4096
- OSC0 /32768
- OSC0 /262144
- CNT0/DLY0/ FSM0 (OUT)
- Ext. Clk. (From matrix)



CNT/DLY BLOCK ON EXAMPLE SLG46826

COUNTER/FSM MODE

Properties

16-bit CNT0/DLY0/FSM0 (MF0)

Multi-function mode:

CNT/DLY

Type:

CNT/DLY

Mode:

Counter/FSM

Counter data:

1

(Range: 1 - 65535)

Output period (typical):

976.563 ns

[Formula](#)

Edge select:

Both

DLY IN init. value:

Bypass the initial

Output polarity:

Non-inverted (OU)

Up signal sync.:

Bypass

Keep signal sync.:

Bypass

Mode signal sync.:

Bypass

FSM SET/RST Selection:

Reset to 0

Connections

Clock:




OSC1

Clock source:

OSC1 Freq.

Clock frequency:

2.048 MHz

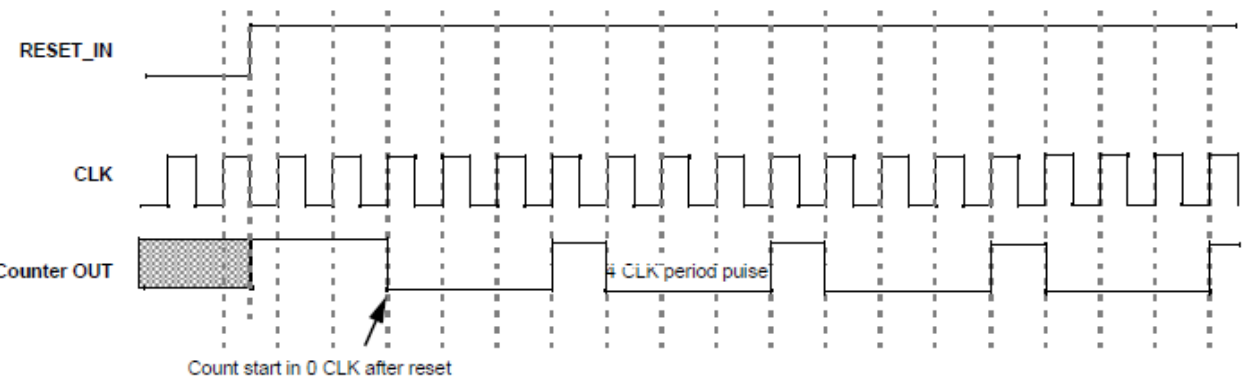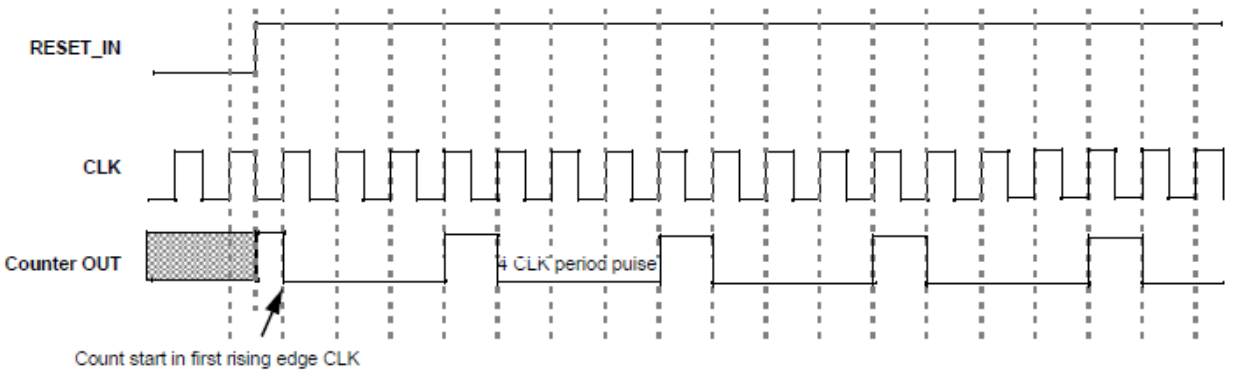 

Bypass

After two dff

Reset to 0

Set to data

CNT/DLY BLOCK ON EXAMPLE SLG46826

ONE SHOT MODE

Properties

8-bit CNT1/DLY1 (MF1)

Multi-function mode: CNT/DLY

Mode: One shot

Counter data: 1
(Range: 1 - 255)

Pulse width (typical): 976.563 ns
[Formula](#)

Edge select: Both

DLY IN init. value: Bypass the initial

Output polarity: Non-inverted (OU)

Up signal sync.: None

Keep signal sync.: None


Mode signal sync.: Bypass

Connections

Clock: OSC1

Clock source: OSC1 Freq.

Clock frequency: 2.048 MHz

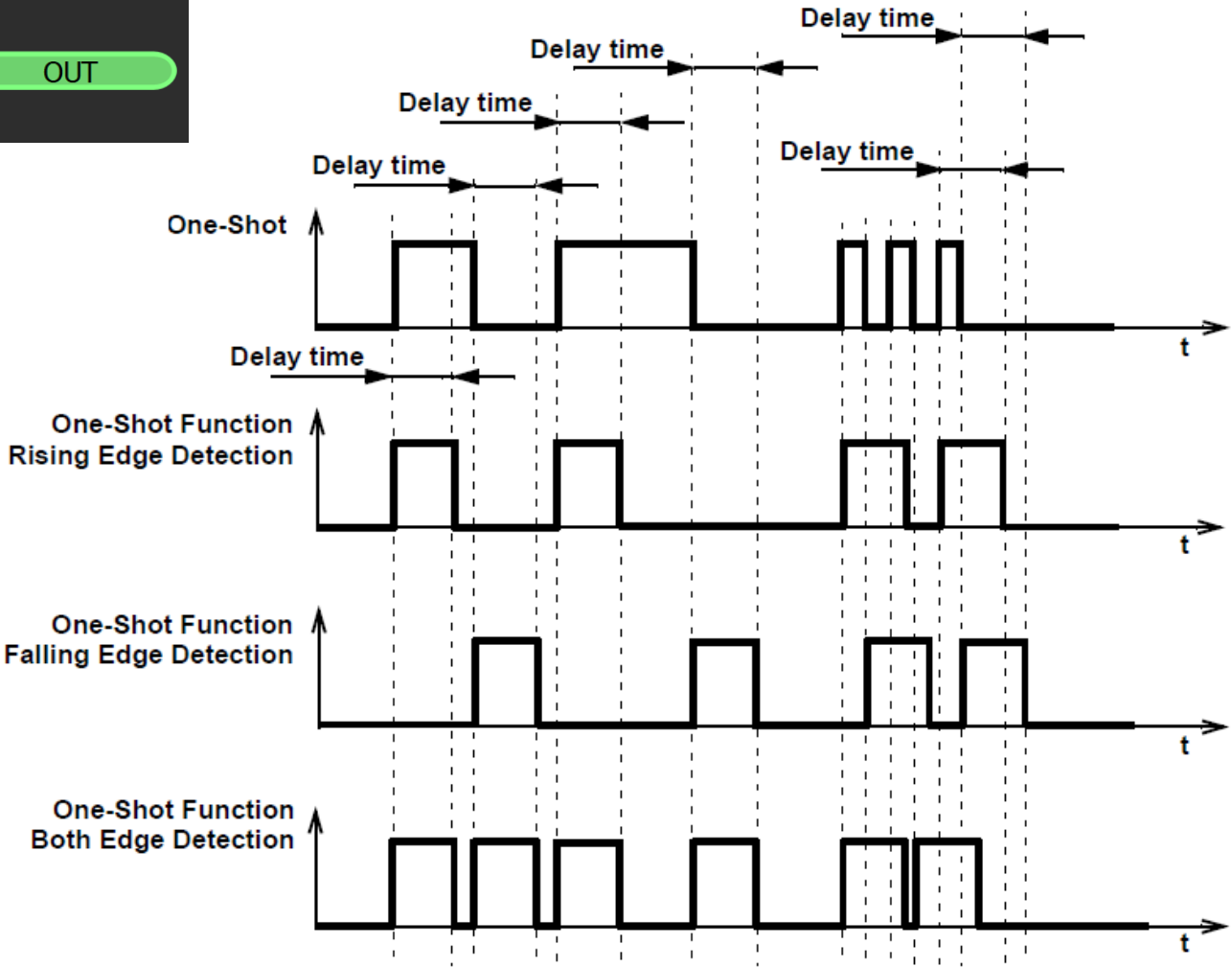

CNT/DLY BLOCK ON EXAMPLE SLG46826

FREQUENCY DETECT MODE

Properties

8-bit CNT1/DLY1 (MF1)

Multi-function mode: CNT/DLY

Mode: Frequency detect

Counter data: 1
(Range: 1 - 255)

Period (typical): 976.563 ns [Formula](#)

Edge select: Both

DLY IN init. value: Bypass the initial

Output polarity: Non-inverted (OU)

Up signal sync.: None

Keep signal sync.: None


Mode signal sync.: Bypass

Connections

Clock: OSC1

Clock source: OSC1 Freq.

Clock frequency: 2.048 MHz

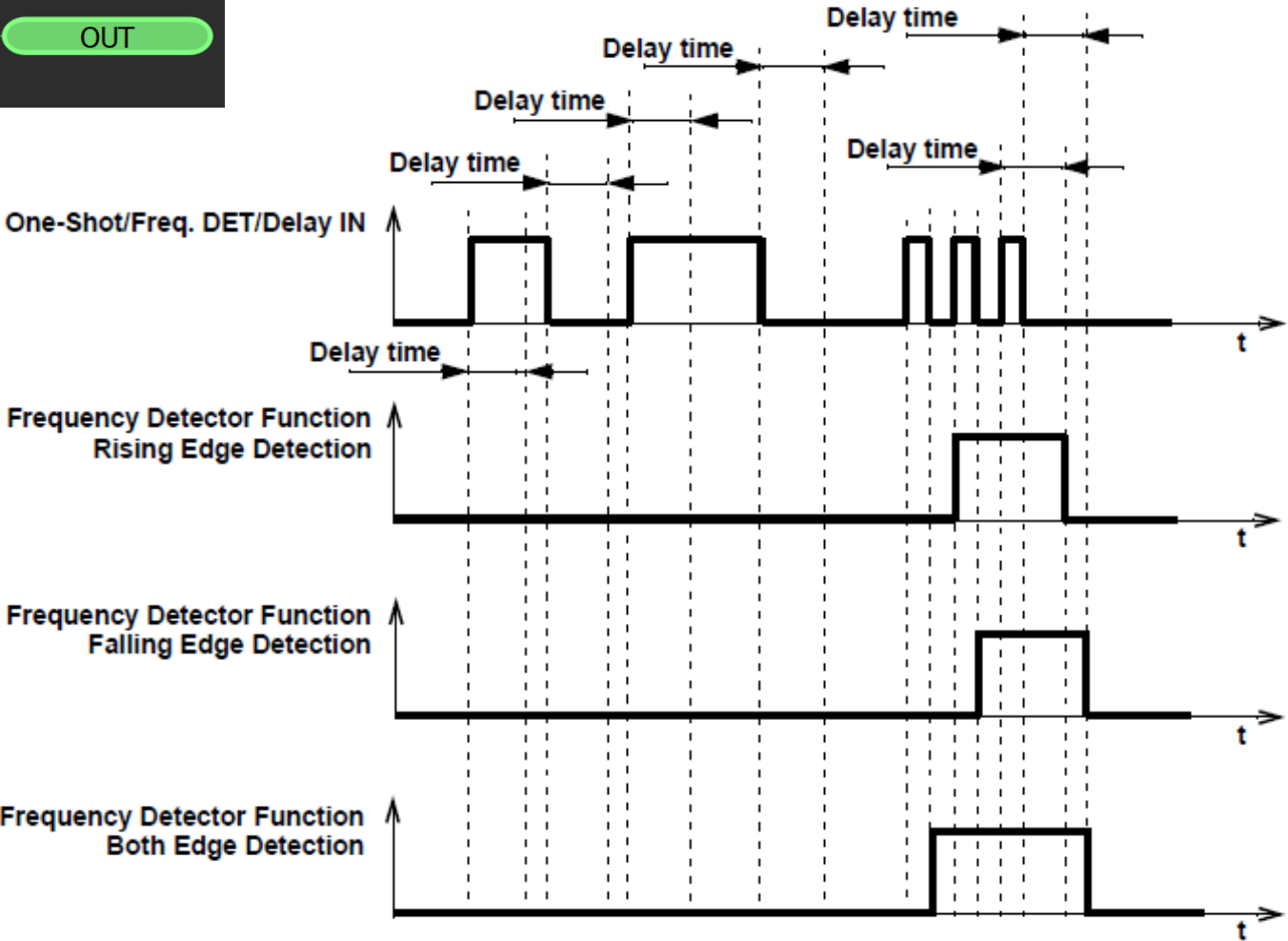

CNT/DLY BLOCK ON EXAMPLE SLG46826

EDGE DETECT MODE

Properties ✕

8-bit CNT1/DLY1 (MF1)

Multi-function mode: CNT/DLY

Mode: Edge detect

~~Counter data: 1~~
(Range: 1 - 255)

Edge select: Both

DLY IN init. value: Bypass the initial

Output polarity: Non-inverted (OU)

Up signal sync.: None

Keep signal sync.: None



Mode signal sync.: Bypass

Connections

Clock: OSC1

Clock source: OSC1 Freq.

Clock frequency: 2.048 MHz

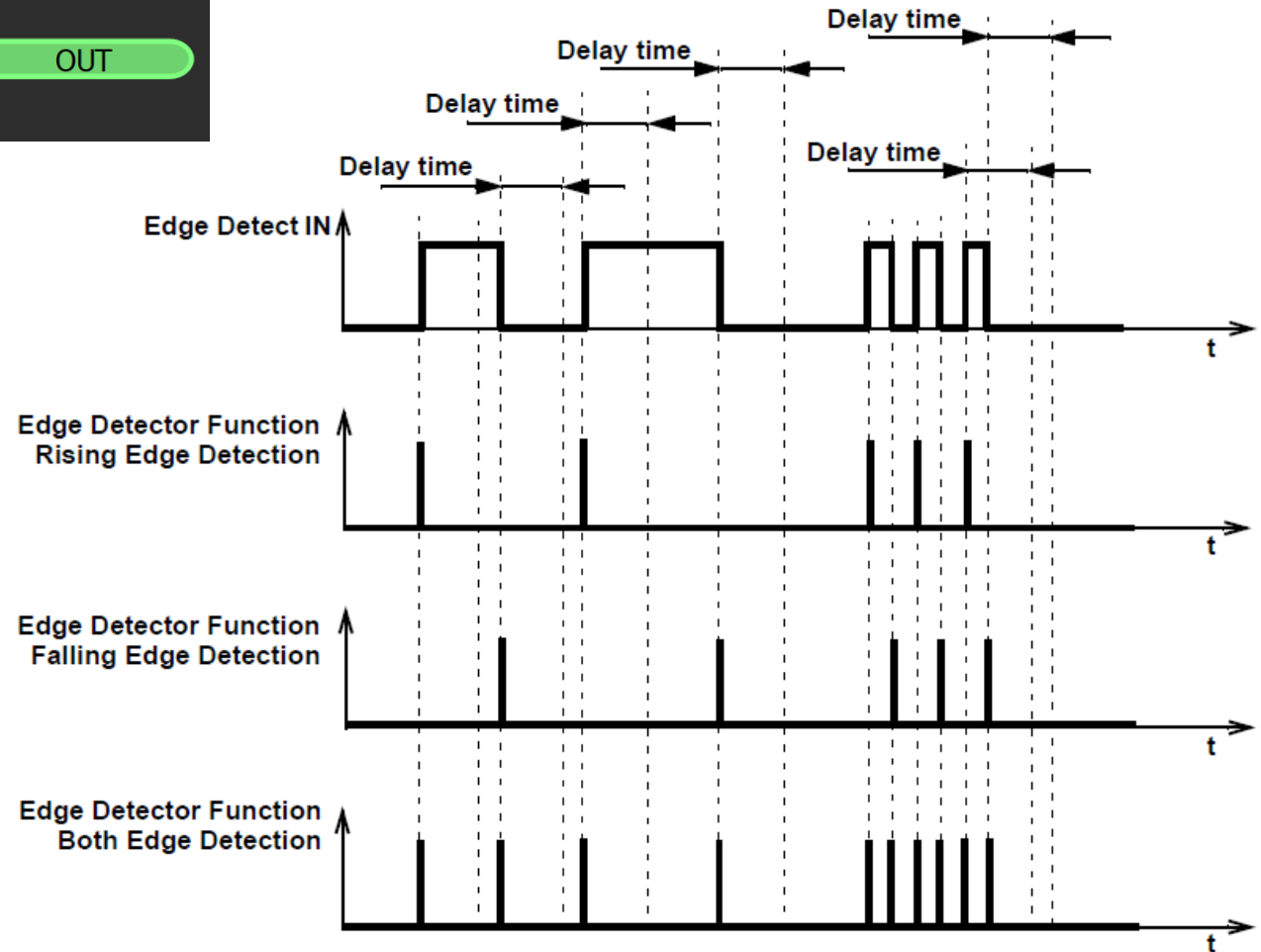 


ШИРОТНО-ІМПУЛЬСНА МОДУЛЯЦІЯ

Що таке PWM?


Широтно-імпульсна модуляція (Pulse Width Modulation, PWM) – це метод управління сигналами шляхом зміни тривалості імпульсів при постійній частоті. Вона широко використовується для:

 - керування потужністю (LEDs, motor, temperature regulation)
- генерації та обробка сигналів (аудіообробка D class, генерація аналогових сигналів)
- енергоефективності в керування живленням (DC-DC, інвертори)
- телекомунікації та зв'язку (модуляція сигналів, інфрачервоні пульти)




PWM DC MOTOR CONTROL TECHNIQUES

PWM SPEED CONTROL

 

 
- The motor speed is determined by the voltage applied to the motor.



- We can change it using PWM to high or low bridge side of the HVPAK.


DC MOTOR CONTROL TECHNIQUES

Supply voltage speed dependency

 

The motor speed is proportional to the HV_OUT average voltage.


Constant Voltage Control

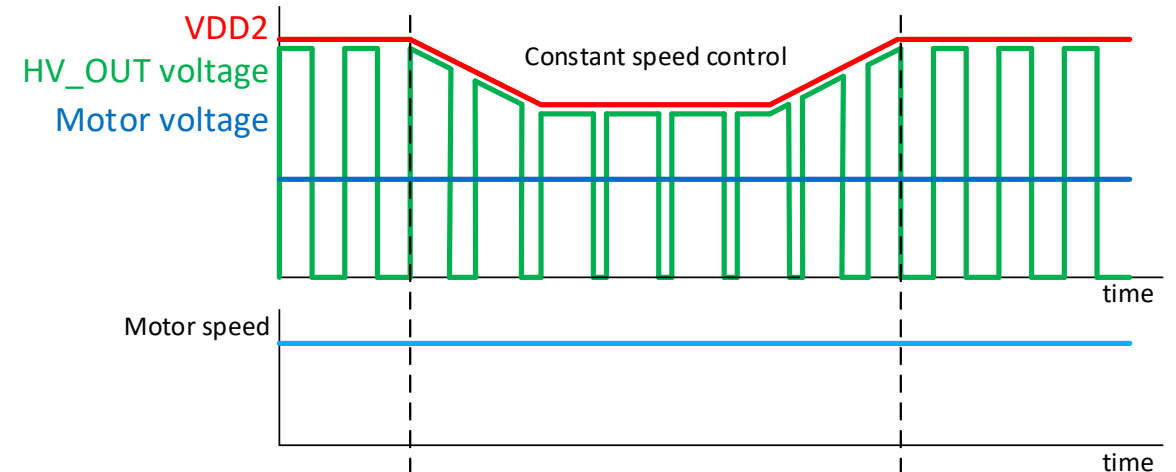

compensation the average voltage on the motor using PWM duty cycle and control motor speed stays constant.

PWM APPLICATION EXAMPLE

PWM LED Control example

 


- Static or dynamic PWM duty cycle control to change LED brightness
- PWM frequency equals 20kHz
- LED connection to VDD or GND
- Open Drain (or Push Pull) outputs
- *For Open Drain (Push Pull) sinking current parameters please refer to datasheet to calculate the resistors R1 and R2



POWER SEQUENCER APPLICATION EXAMPLE

6 Rails Power Sequencer

 


- Create different power up/down sequences
- Up and Down inputs to start and finish sequencing
- Different time between the rails



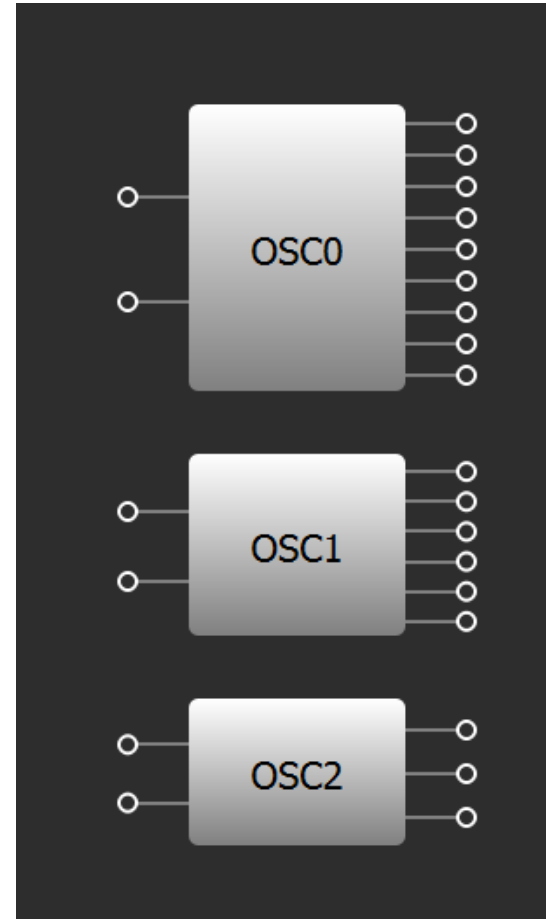2.0 x 3.0 mm STQFN
20-pin package

OSCILLATORS...

- Most GreenPAK devices have at least two oscillators
- Newest devices have three oscillators
- SLG46824/826 have three oscillators
 - 2kHz low speed, low power oscillator
 - 2MHz medium speed
 - 25MHz high speed
- *Auto-power on* option allows you to turn off the oscillator when the clock is not needed
 - Great way to save power
- Oscillator outputs have several pre-dividers to allow you flexibility in clocking



[Renesas.com](https://www.renesas.com)